

Sample Problem from Chapter 10

Consider the small-signal amplifier shown in Figure 1. Assume $V_{CC} = 24\text{ V}$, $R_S = 1.5\text{ k}\Omega$, $R_1 = 8.6\text{ k}\Omega$, $R_2 = 200\text{ k}\Omega$, $R_C = 5\text{ k}\Omega$, $R_L = 2\text{ k}\Omega$, $\beta = 75$, and $r_e = 750\ \Omega$.

- Draw the DC bias circuit and prove that the BJT operates in the active region.
- Draw the small-signal equivalent circuit and find the voltage gain of the amplifier.

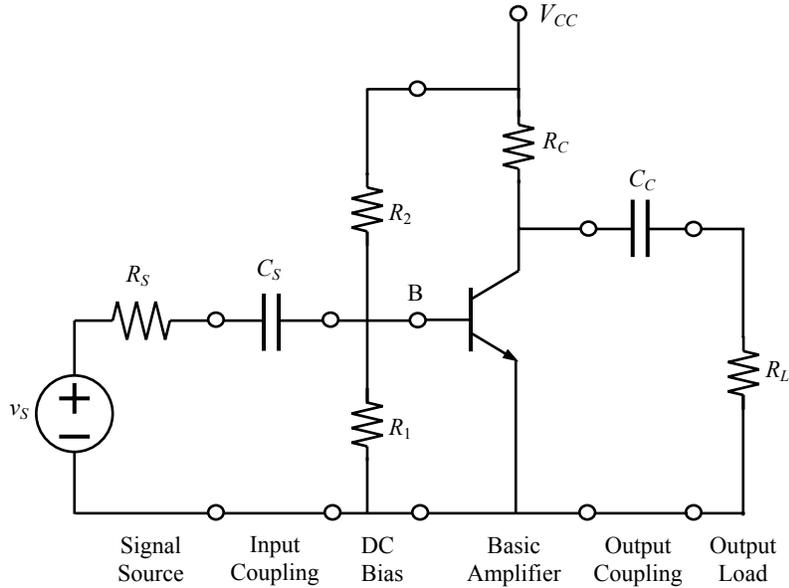


Figure 1 A stage of an amplifier circuit.

Solution: A DC current is supplied to the BJT base by the voltage divider R_1 and R_2 . The coupling capacitors act as blocks to the DC current; therefore the equivalent circuit at DC is as shown in Figure 2 (a). Although, practically there is one power supply, the V_{CC} symbol can be replaced with two voltage sources. The circuit in Figure 2 (a) can further be reduced to the circuit shown in Figure 2 (b) by converting the voltage divider to a Thevenin equivalent circuit (Thevenin theorem can be found in your textbook: pp. 102-109). The symbol V_{BB} is used for the open-circuit voltage at the base of the BJT.

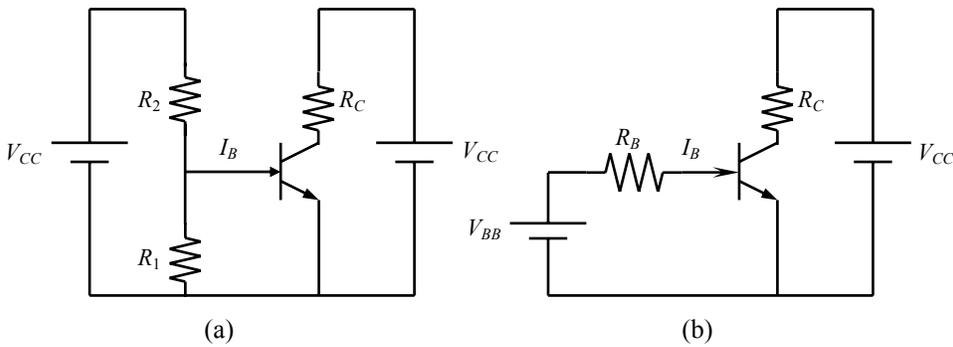


Figure 2 (a) DC bias circuit. (b) Equivalent of the input portion.

Step One: The DC analysis

The open-circuit base DC bias voltage is

	$V_{BB} = 24 \times \frac{8.6}{8.6 + 200} = 0.99 \text{ V}$	
--	---	--

The DC output impedance of the bias network is

	$R_B = 8.6 // 200 = 8.25 \text{ k}\Omega$	
--	---	--

A silicon transistor requires a threshold voltage of $V_{BE} = 0.7 \text{ V}$ to turn ON the base-emitter junction, therefore

	$I_B = \frac{V_{BB} - 0.7}{R_B} = \frac{0.99 - 0.7}{8.25 \text{ k}\Omega} = 35.1 \mu\text{A}$	
	$I_C = \beta I_B = 75 \times 35.1 \times 10^{-6} = 2.63 \text{ mA}$	

Now consider the closed loop path in the output circuit of the amplifier and apply KVL in order to find the collector-emitter voltage V_{CE} .

	$-V_{CC} + I_C R_C + V_{CE} = 0$	
	$V_{CE} = 24 - 5 \times 2.63 = 10.8 \text{ V}$	

Therefore, the BJT is operating in the active region.

Step Two: AC Analysis

All capacitors are replaced by short circuit. The voltage source v_s and its internal resistance R_S are replaced by a current source (v_s/R_S) according to Source Transformation theorem (see page 112 of the textbook)

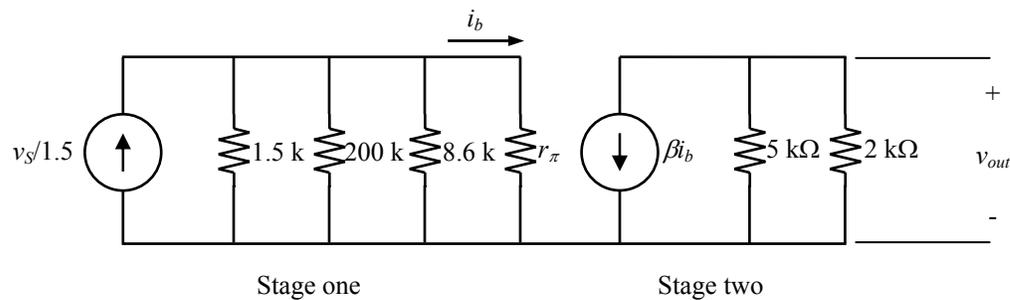


Figure 3: Small-signal circuit of the BJT amplifier.

Consider the circuit in stage one, first.

- Let us find the equivalent resistance of the four resistors: 1.5, 200, 8.6, and 0.75

$$\frac{1}{R_T} = \frac{1}{1.5} + \frac{1}{200} + \frac{1}{8.6} + \frac{1}{0.75}$$

$$R_T = 0.472 \text{ k}\Omega$$

Stage one circuit will turn into the following circuit

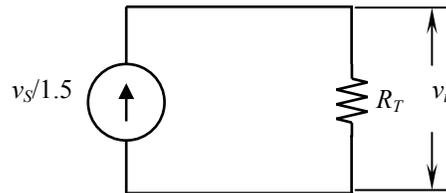


Figure 4: Equivalent circuit of stage-one circuit.

$$v_i = \frac{v_S}{1.5} \times R_T = 0.314 v_S$$

This value of v_i is same across each element in the circuit of Figure 3. Now, apply ohm's law to find i_b

$$i_b = \frac{v_i}{r_\pi} = \frac{0.314 v_S}{0.75} = 0.416 v_S$$

Now, consider stage two circuit

$$v_{out} = -75 i_b \times (2//5) = -75 \times 0.416 v_S \times 1.42 = -44.6 v_S$$

Accordingly, the gain is $v_{out}/v_S = -44.6$. The (-) sign is an indication for the counterclockwise direction of current in stage-two circuit.